

Branch, Node and Loop

- ❑ A branch represents a **single element** such as a voltage or current source or a resistor.
- ❑ A node is the point of **interconnection** between two or more branches.
- ❑ A loop is a **closed path** in a circuit.

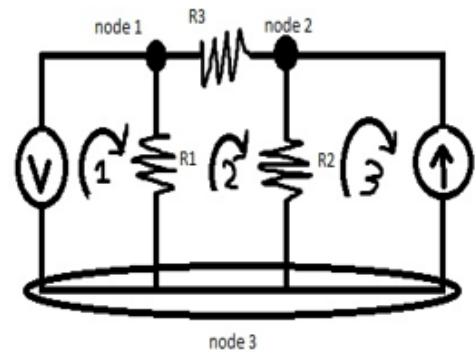


Fig: A circuit for Branch, Node and loop analysis

Short Circuit


If the resistor is a **perfect conductor** (or a short circuit).

$$R = 0 \, \Omega,$$

then

$$v = IR = 0 \, V$$

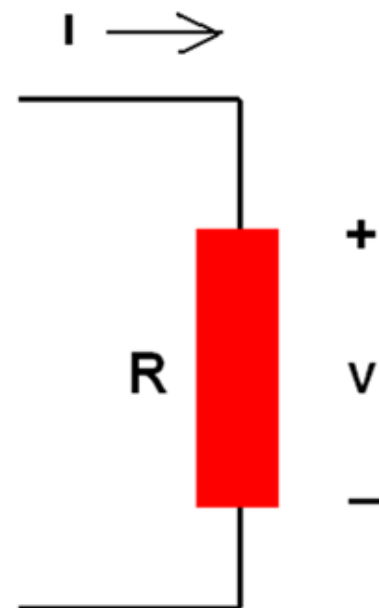No matter how much current is flowing through the resistor



Open Circuit

If the resistor is a perfect insulator, $R = \infty \Omega$

Then no matter how much voltage is applied to (or dropped across) the resistor.

